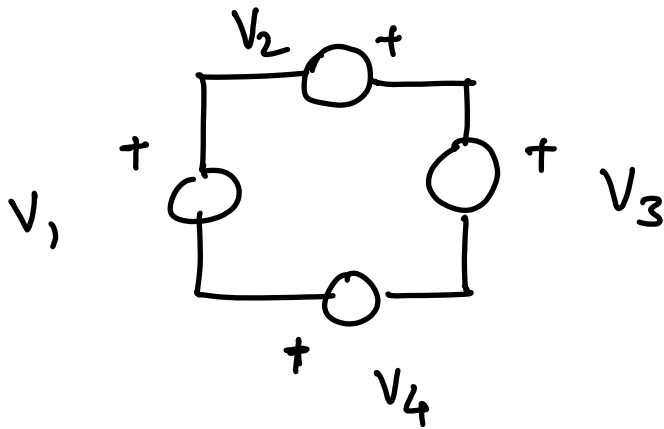


2.3 Kirchhoff's laws

(a) Voltage law

Sum of voltages in a loop adds to zero

$$\sum_{i=1}^n V_i = 0$$




$$\text{KVL : } \sum_{i=1}^4 V_i = 0$$

$$V_1 + V_2 - V_3 + V_4 = 0$$

(b) Current law:


Sum of currents at a node add to zero.

$$\sum_{i=1}^N I_i = 0$$

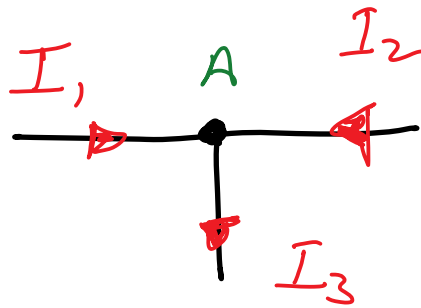


At node A: $+I_1 + I_2 - I_3 = 0$

Series circuit

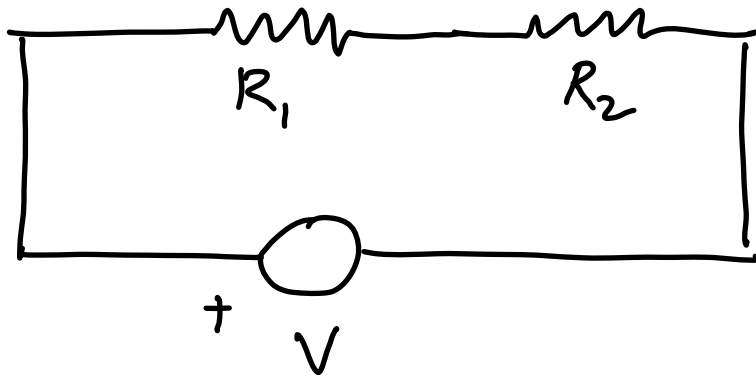

Compute the current in the circuit

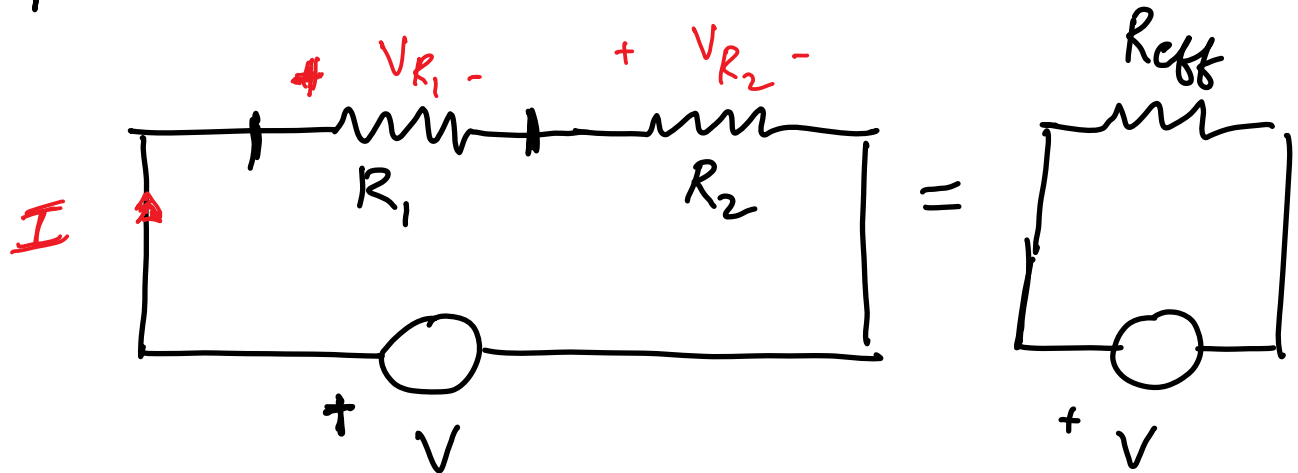

$$\text{KVL: } \sum V_i = 0$$

$$V - V_{R_1} - V_{R_2} = 0$$

$$V - IR_1 - IR_2 = 0$$

$$I = \frac{V}{R_1 + R_2} = \frac{V}{R_{eff}}$$



$$R_{\text{eff}} = R_1 + R_2$$

$$V_{R_1} = I R_1 = \left(\frac{V}{R_1 + R_2} \right) R_1 = \frac{R_1}{R_1 + R_2} V$$

$$V_{R_2} = \frac{R_2}{R_1 + R_2} V$$

Voltage divider

HW

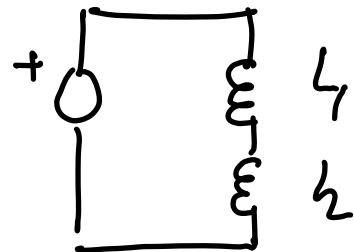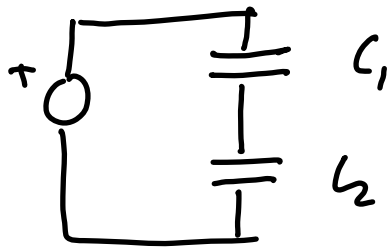


Compute effective capacitance & inductance


$$C_{\text{eff}} = \frac{C_1 C_2}{C_1 + C_2}$$

$$L_{\text{eff}} = L_1 + L_2$$

(b) Parallel circuit

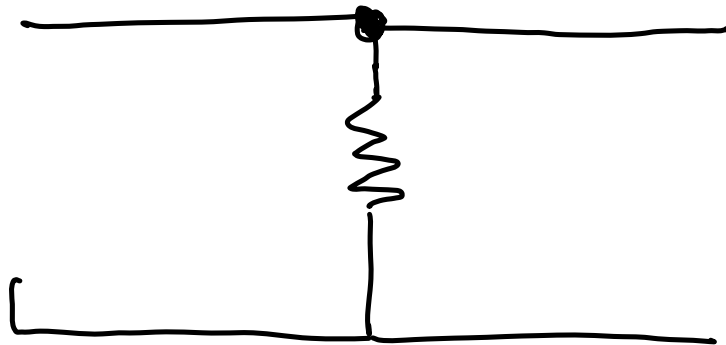

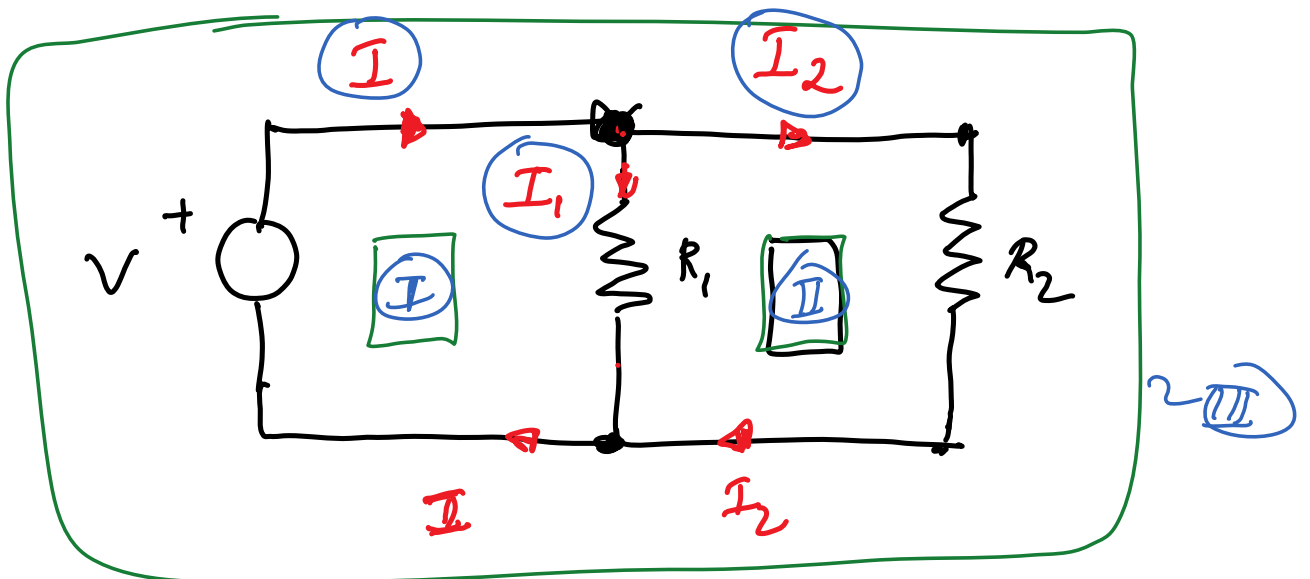Compute the current and effective resistance.



KVL: $\sum V = 0$

$$\textcircled{I} \quad V - I_1 R_1 = 0 ; \quad V - I_2 R_2 = 0 \quad \textcircled{II}$$

$$I_1 R_1 - I_2 R_2 = 0 \quad \sim \quad \textcircled{III}$$

$$\text{KCL: } I - I_1 - I_2 = 0$$

$$I = I_1 + I_2$$

Summary

$$I_1 R_1 = V \Rightarrow I_1 = V/R_1$$

$$I_2 R_2 = V \Rightarrow I_2 = V/R_2$$

$$I_1 + I_2 - I = 0 \Rightarrow I = \frac{V}{R_1} + \frac{V}{R_2}$$


$$I = V \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$

$$\frac{V}{I} = R_{\text{eff}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{V}{R_1} = \left[\left(\frac{R_1 R_2}{R_1 + R_2} \right) I \right] \frac{1}{R_1}$$


$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I$$
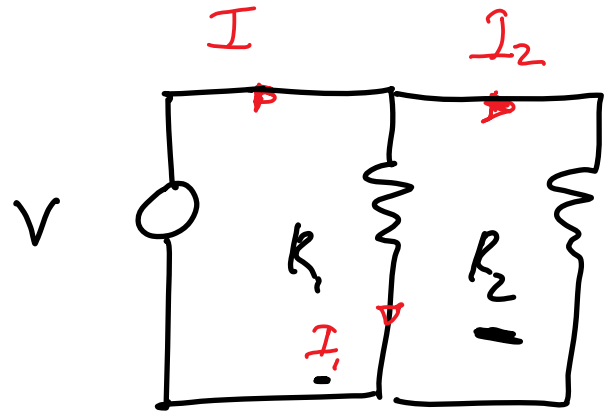
$$I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I$$




Current Divider Circuit

HW

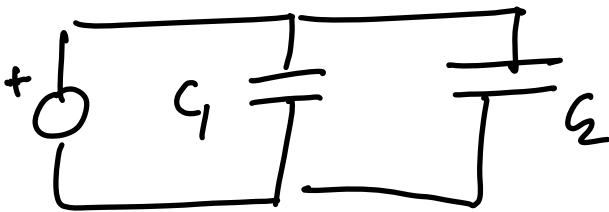


$$C_{\text{eff}} = C_1 + C_2$$

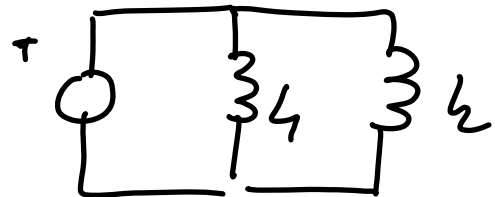

$$L_{\text{eff}} = \frac{L_1 L_2}{L_1 + L_2}$$

Example:

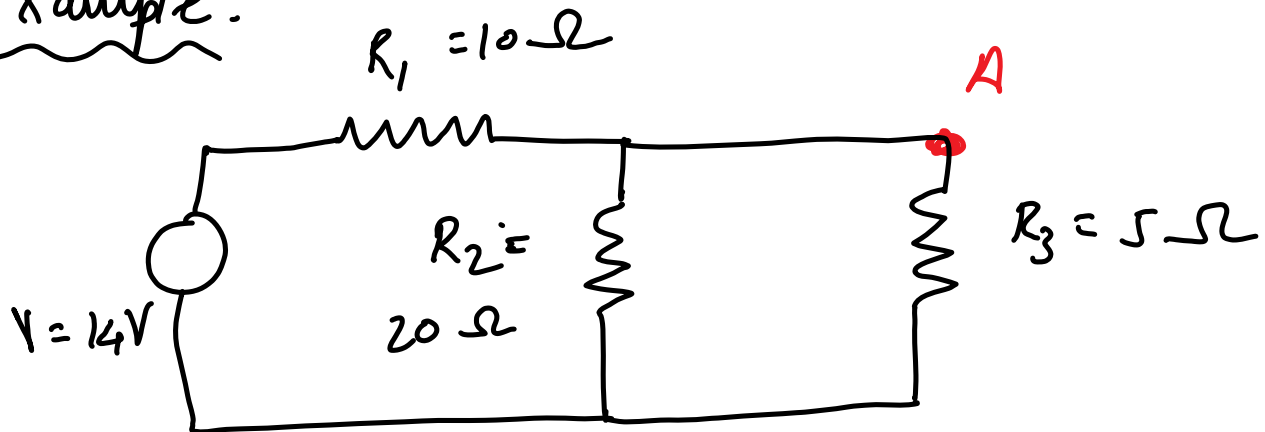

- (i) Compute equivalent resistance
- (ii) Compute the currents through R_1, R_2, R_3
- (iii) Compute voltage at node A.


(i) $R_{23} = \frac{R_2 R_3}{R_2 + R_3} \Rightarrow$

R_1 R_{23}

$R_{eff} = R_1 + R_{23}$


R_{eff}
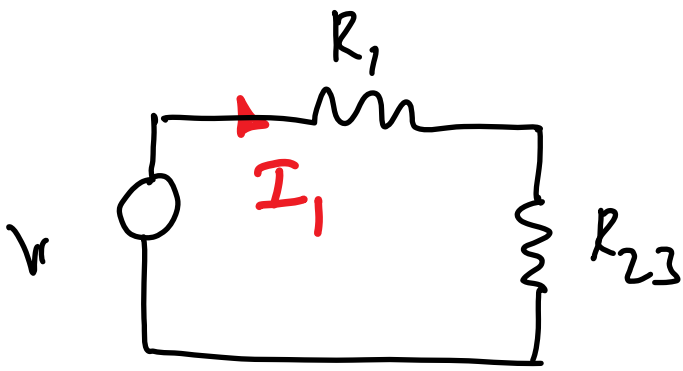
$$R_{eff} = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 14 \Omega$$



$$I_1 = \frac{V}{R_{\text{eff}}} = \frac{14}{14}$$

$$I_1 = 1 \text{ A}$$

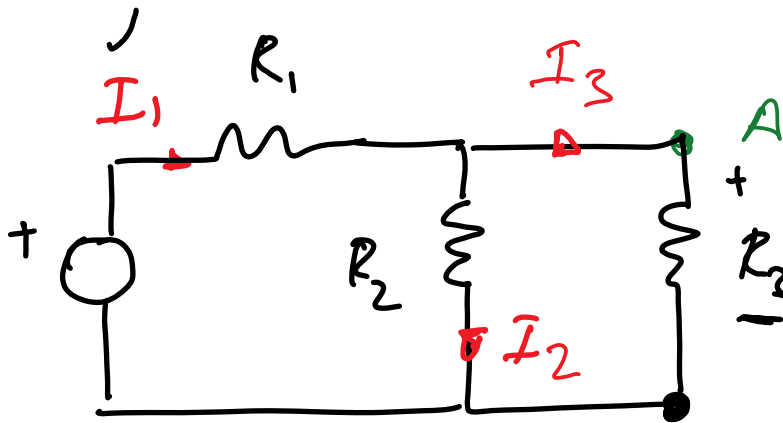

$$I_2 = \frac{R_3}{R_2 + R_3} I_1 \quad ; \quad I_3 = \frac{R_2}{R_2 + R_3} I_1$$


$$I_2 = 0.2 \text{ A}$$

$$I_3 = 0.8 \text{ A}$$

$$(c) \quad V_A = V_{R_3} = I_3 R_3 = 0.8 (5) = 4 \text{ V}$$

$$V_A = 4 \text{ V}$$

Example:


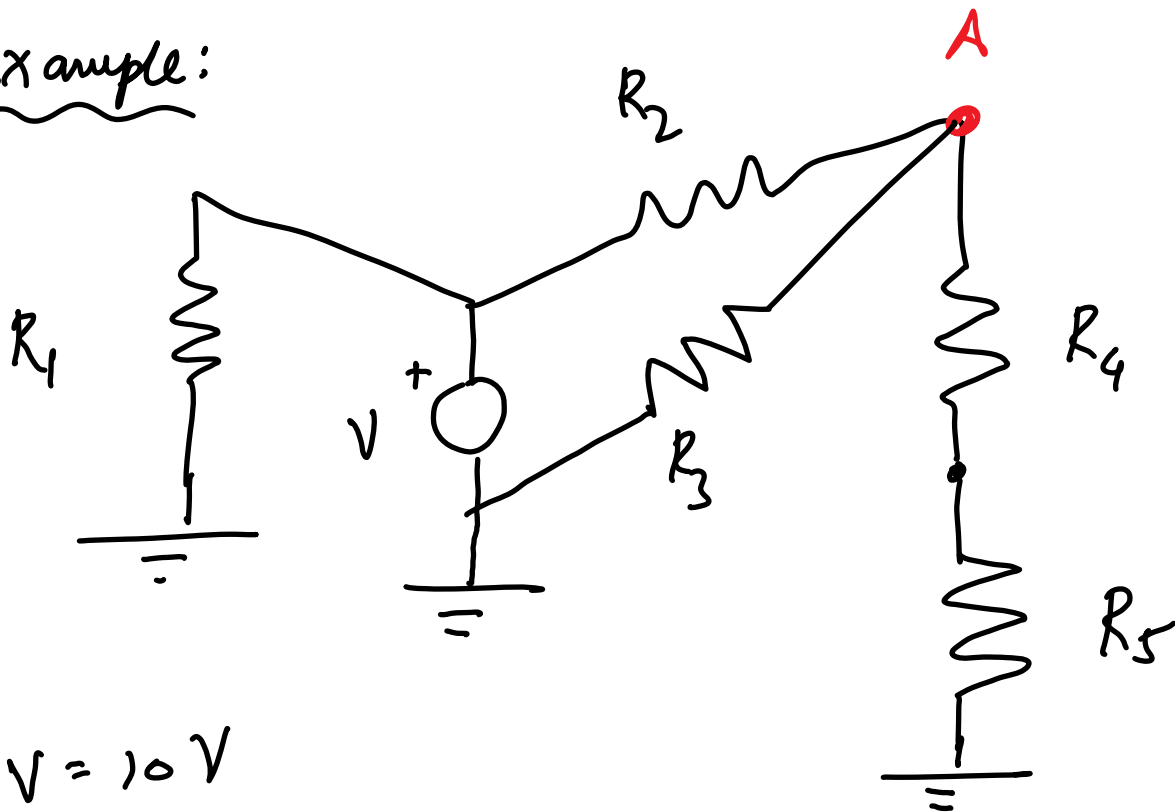


$$V = 10\text{ V}$$

$$R_1 = 1\text{ k}\Omega, R_2 = 2\text{ k}\Omega, R_3 = 3\text{ k}\Omega$$


$$R_4 = 4\text{ k}\Omega; R_5 = 1\text{ k}\Omega$$

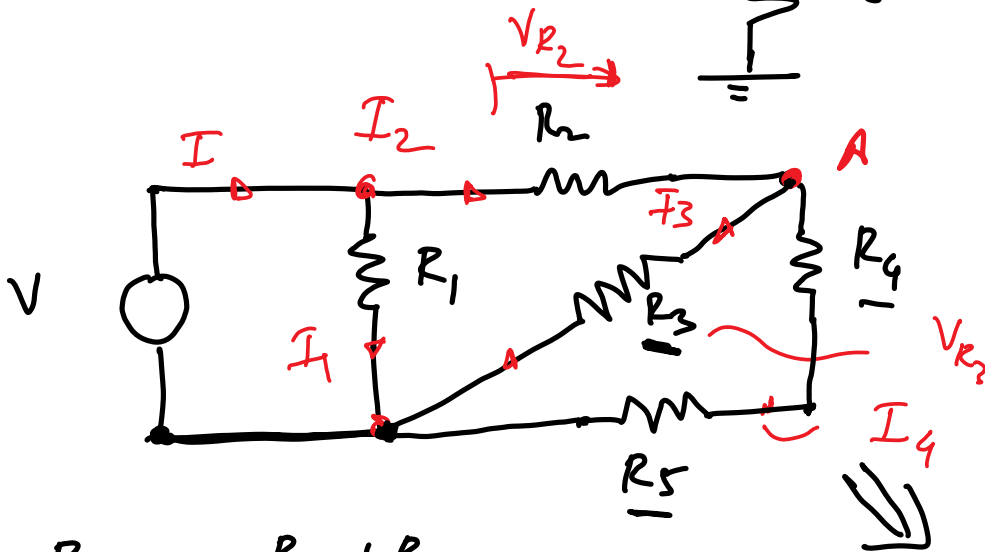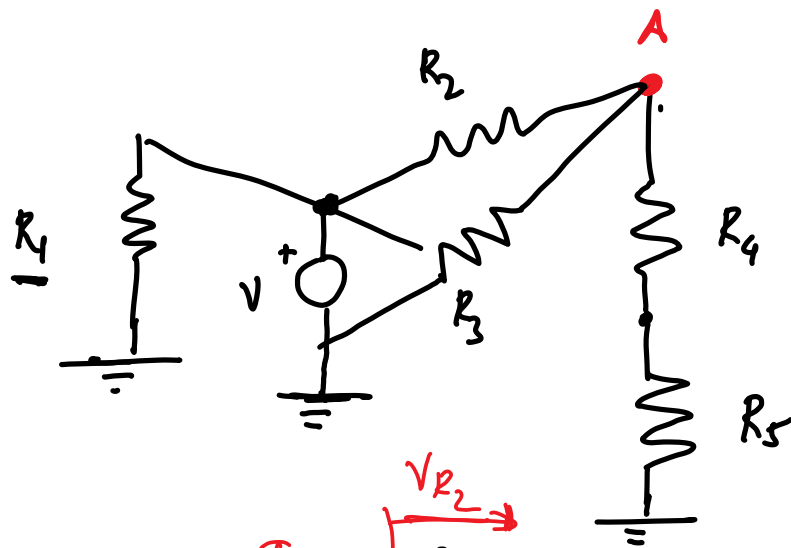- Compute
- (i) Equivalent resistance
 - (ii) Voltage at node A
 - (iii) Current through resistor R_5



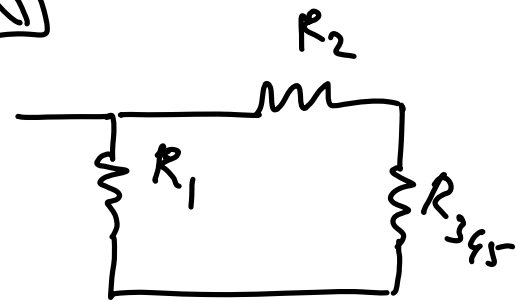(i) $R_{45} = R_4 + R_5$

$$R_{345} = \frac{R_3 R_{45}}{R_3 + R_{45}}$$




$$R_{2345} = R_2 + R_{345}$$


$$R_{\text{eff}} = \frac{R_1 R_{2345}}{R_1 + R_{2345}}$$

$R_{\text{eff}} = 0.795 \text{ k}\Omega$

$$V_A = I_2 R_2 + I_3 R_3$$

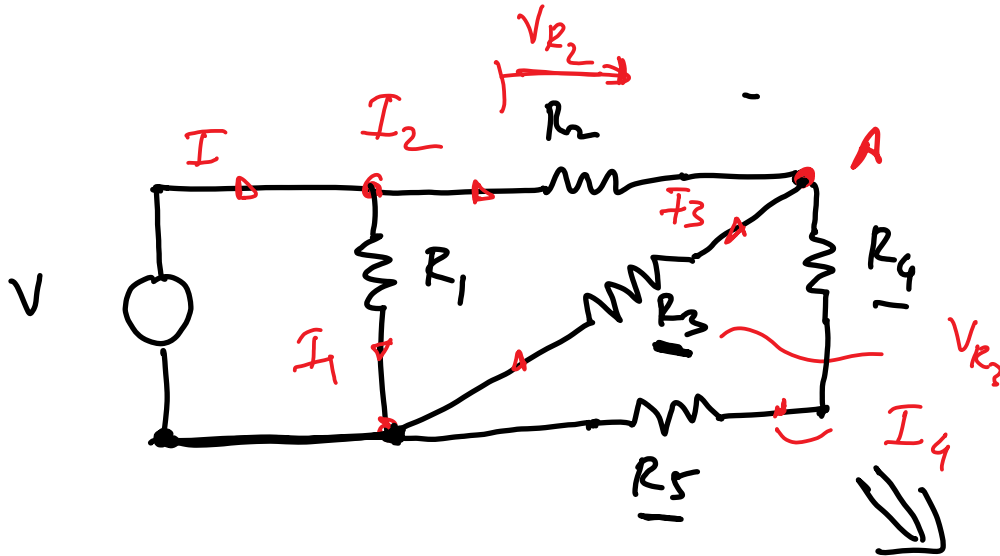

$$I = \frac{V}{R_{\text{eff}}}$$

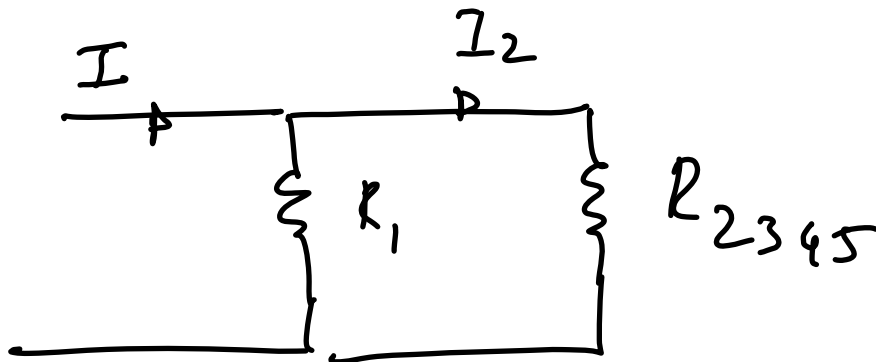

$$I_2 = \left(\frac{R_1}{R_1 + R_{2345}} \right) I$$



$$I_3 = \frac{R_5}{R_3 + R_5} I_2$$

$$R_3 + R_5$$

$$V_A = 4.84 \text{ V}$$

$$(iii) \quad I_4 = \frac{R_3}{R_3 + R_5} I_2$$

$$I_4 = 0.97 \text{ mA}$$